

DECODER IN VERILOG

LAB # 08



Fall 2023

CSE-304L Computer Organization and Architecture Lab

Submitted by: **Ali Asghar**

Registration No.: **21PWCSE2059**

Class Section: **C**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Submitted to:

Dr. Bilal Habib

Date:

17th December 2023


Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

ASSESSMENT RUBRICS COA LABS

LAB REPORT ASSESSMENT				
Criteria	Excellent	Average	Nil	Marks Obtained
1. Objectives of Lab	All objectives of lab are properly covered [Marks 10]	Objectives of lab are partially covered [Marks 5]	Objectives of lab are not shown [Marks 0]	
2. MIPS instructions with Comments and proper indentations.	All the instructions are well written with comments explaining the code and properly indented [Marks 20]	Some instructions are missing are poorly commented code [Marks 10]	The instructions are not properly written [Marks 0]	
3. Simulation run without error and warnings	The code is running in the simulator without any error and warnings [Marks 10]	The code is running but with some warnings or errors. [Marks 5]	The code is written but not running due to errors [Marks 0]	
4. Procedure	All the instructions are written with proper procedure [Marks 20]	Some steps are missing [Marks 10]	steps are totally missing [Marks 0]	
5. OUTPUT	Proper output of the code written in assembly [Marks 20]	Some of the outputs are missing [Marks 10]	No or wrong output [Marks 0]	
6. Conclusion	Conclusion about the lab is shown and written [Marks 20]	Conclusion about the lab is partially shown [Marks 10]	Conclusion about the lab is not shown[Marks0]	
7. Cheating			Any kind of cheating will lead to 0 Marks	
<p style="text-align: center;">Total Marks Obtained: _____</p> <p style="text-align: center;">Instructor Signature: _____</p>				

 Task 1:

Implement 2X4 Decoder using gate level modeling in Verilog.



Code:

DUT Code:


```
tb_task2.v x task2.v x task3.v x 2x4_Decoder.v x tb_2x4_Decoder.v x 3x8_Decoder.v x tb_3x_Decoder.v
1  module Decoder_2x4 (A, B, E, I);
2
3      input A;
4      input B;
5      input E;
6      output [3:0] I;
7
8      wire nA;
9      wire nB;
10
11     not n1 (nA, A);
12     not n2 (nB, B);
13
14     and a1 (I[0], nA, nB, E);
15     and a2 (I[1], nA, B, E);
16     and a3 (I[2], A, nB, E);
17     and a4 (I[3], A, B, E);
18 endmodule
19
```

Test bench Code:

```
tb_task2.v x task2.v x task3.v x 2x4_Decoder.v x tb_2x4_Decoder.v x 3x8_Decoder.v x tb_3x_Decoder.v x task3.v x tb_ta
1 module tb_Decoder_2x4();
2
3     reg A;
4     reg B;
5     reg E;
6     wire [3:0] I;
7
8     Decoder_2x4 my_2x4_Decoder(A,B,E,I);
9
10    initial begin
11        A = 0;
12        B = 0;
13        E = 0;
14        $display("%b %b %b %b", A , B, E, {I[0], I[1], I[2], I[3]});
15        #10
16
17        A = 0;
18        B = 0;
19        E = 1;
20        $display("%b %b %b %b", A , B, E, {I[0], I[1], I[2], I[3]});
21        #10
22
23        A = 0;
```

```
tb_task2.v x task2.v x task3.v x 2x4_Decoder.v x tb_2x4_Decoder.v x 3x8_Decoder.v x tb_3x_Decoder.v x task3.v x tb_ta
21    #10
22
23    A = 0;
24    B = 1;
25    E = 1;
26    #10
27
28    $display("%b %b %b %b", A , B, E, {I[0], I[1], I[2], I[3]});
29    A = 1;
30    B = 0;
31    E = 1;
32    $display("%b %b %b %b", A , B, E, {I[0], I[1], I[2], I[3]});
33    #10
34
35    A = 1;
36    B = 1;
37    E = 1;
38    $display("%b %b %b %b", A , B, E, {I[0], I[1], I[2], I[3]});
39
40    end
41
42    endmodule
```

Output:

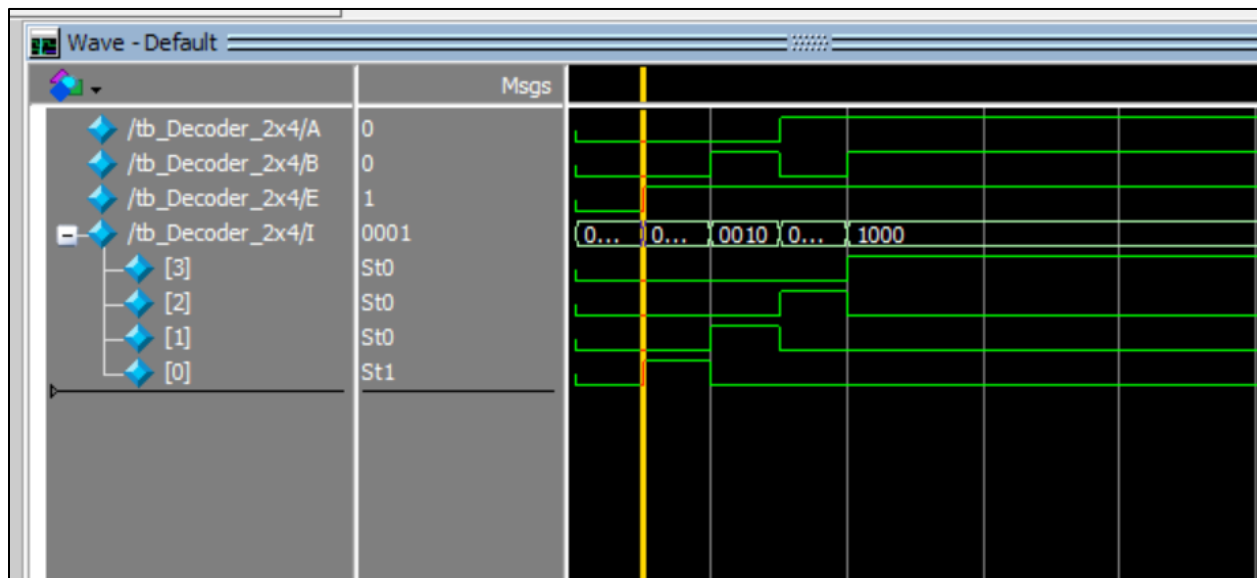

Task 2:

Implement 3X8 Decoder using gate level modeling in Verilog.

Code:

DUT Code:

```
task2.v task3.v 2x4_Decoder.v tb_2x4_Decoder.v 3x8_Decoder.v tb_3x_Decoder.v
module Decoder_3x8 (A, B, C, E, I);
    input A;
    input B;
    input C;
    input E;
    output [7:0] I;

    wire nA;
    wire nB;
    wire nC;
```

```

12     not n1(nA, A);
13     not n2(nB, B);
14     not n3(nC, C);
15
16     and a1(I[0], nA, nB, nC, E);
17     and a2(I[1], nA, nB, C, E);
18     and a3(I[2], nA, B, nC, E);
19     and a4(I[3], nA, B, C, E);
20     and a5(I[4], A, nB, nC, E);
21     and a6(I[5], A, nB, C, E);
22     and a7(I[6], A, B, nC, E);
23     and a8(I[7], A, B, C, E);
24
25 endmodule

```

Test bench Code:

```

1  module tb_Decoder_3x8();
2      reg A;
3      reg B;
4      reg C;
5      reg E;
6      wire [7:0] I;
7
8      Decoder_3x8 my_3x8_Decoder(A,B,C,E,I);
9
10     initial begin
11
12         A = 1;
13         B = 0;
14         C = 1;
15         E = 0;
16         $display("%b %b %b %b %b", A, B, C, E, {I[0], I[1], I[2], I[3], I[4], I[5], I[6], I[7]})
17         #10
18
19         A = 0;
20         B = 0;
21         C = 1;
22         E = 1;

```

```

tb_task2.v tb_task2.v tb_task3.v 2x4_Decoder.v tb_3x_Decoder.v tb_2x4_Decoder.v 3x8_Decoder.v task3.v tb_task3.v task4.v tb_task4.v
22     E = 1;
23     $display("%b %b %b %b %b", A , B, C, E, {I[0], I[1], I[2], I[3], I[4], I[5], I[6], I[7]})
24     #10
25
26     A = 0;
27     B = 1;
28     C = 0;
29     E = 1;
30     $display("%b %b %b %b %b", A , B, C, E, {I[0], I[1], I[2], I[3], I[4], I[5], I[6], I[7]})
31     #10
32
33     A = 0;
34     B = 1;
35     C = 1;
36     E = 1;
37     $display("%b %b %b %b %b", A , B, C, E, {I[0], I[1], I[2], I[3], I[4], I[5], I[6], I[7]})
38
39     A = 1;
40     B = 0;
41     C = 0;
42     E = 1;
43     $display("%b %b %b %b %b", A , B, C, E, {I[0], I[1], I[2], I[3], I[4], I[5], I[6], I[7]})

```

```

tb_task2.v tb_task2.v tb_task3.v 2x4_Decoder.v tb_3x_Decoder.v tb_2x4_Decoder.v 3x8_Decoder.v task3.v tb_task3.v task4.v tb_task4.v
44     #10
45
46     A = 1;
47     B = 0;
48     C = 1;
49     E = 1;
50     $display("%b %b %b %b %b", A , B, C, E, {I[0], I[1], I[2], I[3], I[4], I[5], I[6], I[7]})
51
52     #10
53     A = 1;
54     B = 1;
55     C = 0;
56     E = 1;
57     $display("%b %b %b %b %b", A , B, C, E, {I[0], I[1], I[2], I[3], I[4], I[5], I[6], I[7]})
58
59     #10
60     A = 1;
61     B = 1;
62     C = 1;
63     E = 1;
64     $display("%b %b %b %b %b", A , B, C, E, {I[0], I[1], I[2], I[3], I[4], I[5], I[6], I[7]})
65


```

```

61     B = 1;
62     C = 1;
63     E = 1;
64     $display("%b %b %b %b %b", A , B, C, E, {I[0], I[1], I[2], I[3], I[4], I[5], I[6], I[7]})
65
66     end
67
68     endmodule
69


```

Output:

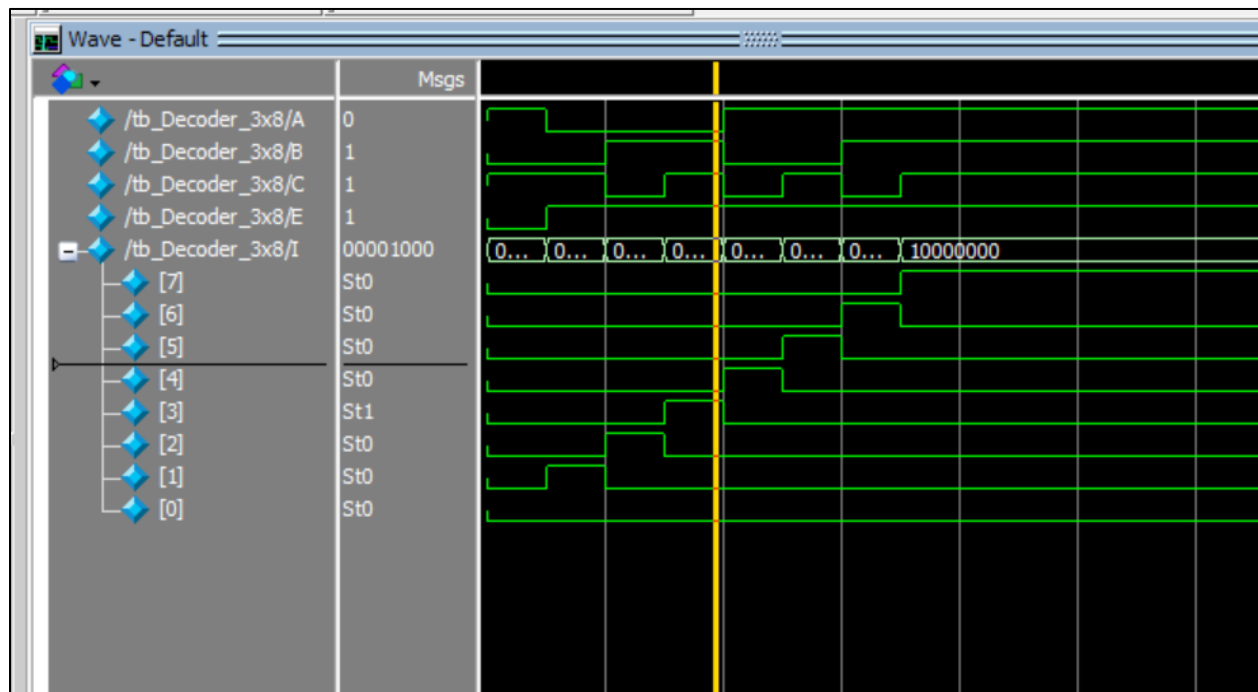

Task 3:

Implement 3X8 Decoder using 2X4 Decoder.

 

Code:


DUT Code:

```
1  module task3(A, B, C, I);
2
3      input A;
4      input B;
5      input C;
6      output [7:0]I;
7
8      wire nA;
9
10     not n1(nA, A);
11
12     Decoder_2x4 d1(B, C, nA, {I[3], I[2], I[1], I[0]});
13     Decoder_2x4 d2(B, C, A, {I[7], I[6], I[5], I[4]});
14
15 endmodule
```

Test bench Code:


Same as task2

Output:

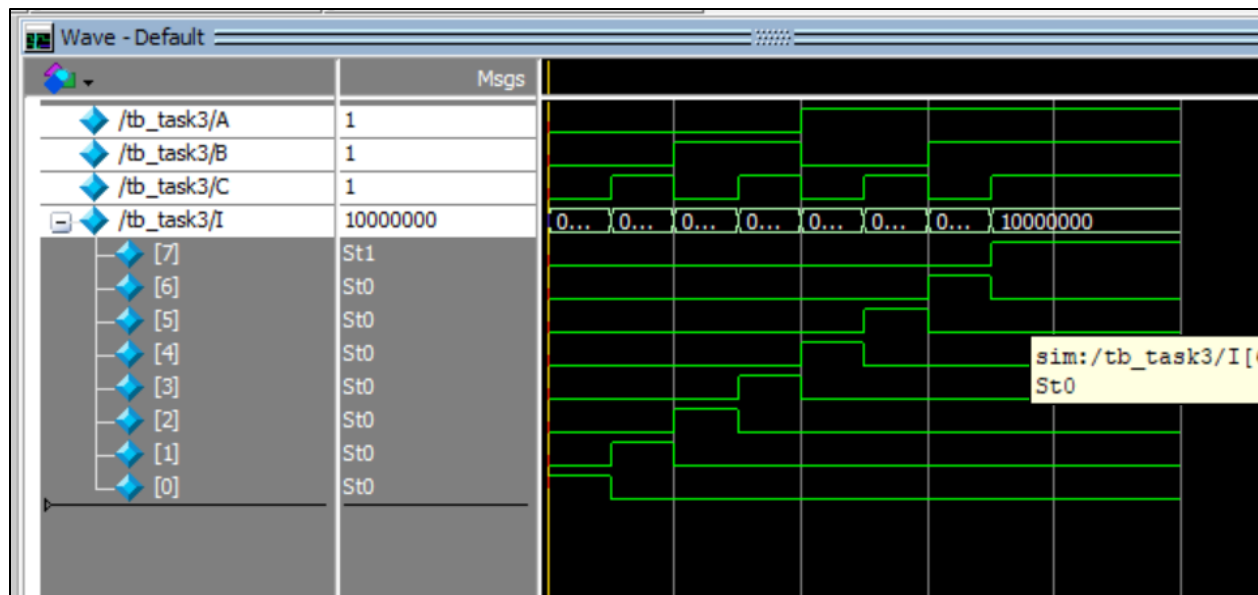

 Task 4:

Implement 4X16 Decoder using 3X8 Decoder.



Code:

DUT Code:


```
tb_task2.v x task2.v x task4.v x task3.v x task3.v x tb_task3.v x 2x4_Decoder.v x tb_3x_Decoder.v x
1  module task4(A, I);
2
3      input [3:0]A;
4
5      output [15:0]I;
6
7      wire nA;
8
9      not n1(nA, A[3]);
10
11      Decoder_3x8 d1(A[2], A[1], A[0], nA, I[7:0]);
12      Decoder_3x8 d2(A[2], A[1], A[0], A[3], I[15:8]);
13
14  endmodule
```

Test bench Code:

```
1  module tb_task4();
2
3      reg [3:0]A;
4      wire [15:0]I;
5
6      task4 my_3x8_Decoder(A,I);
7
8      initial begin
9          A = 4'b0001;
10         #10
11
12         A = 4'b0010;
13         #10
14
15         A = 4'b0011;
16         #10
17
18         A = 4'b0100;
19         #10
20
21         A = 4'b0101;
22         #10
23
```

```
24     A = 4'b0110;  
25     #10  
26     A = 4'b0111;  
27     #10  
28     A = 4'b1000;  
29     #10  
30  
31     A = 4'b1001;  
32     #10  
33  
34     A = 4'b1010;  
35     #10  
36  
37     A = 4'b1011;  
38     #10  
39  
40     A = 4'b1110;  
41     #10  
42  
43     A = 4'b1111;  
44     end  
45 endmodule
```

Output:

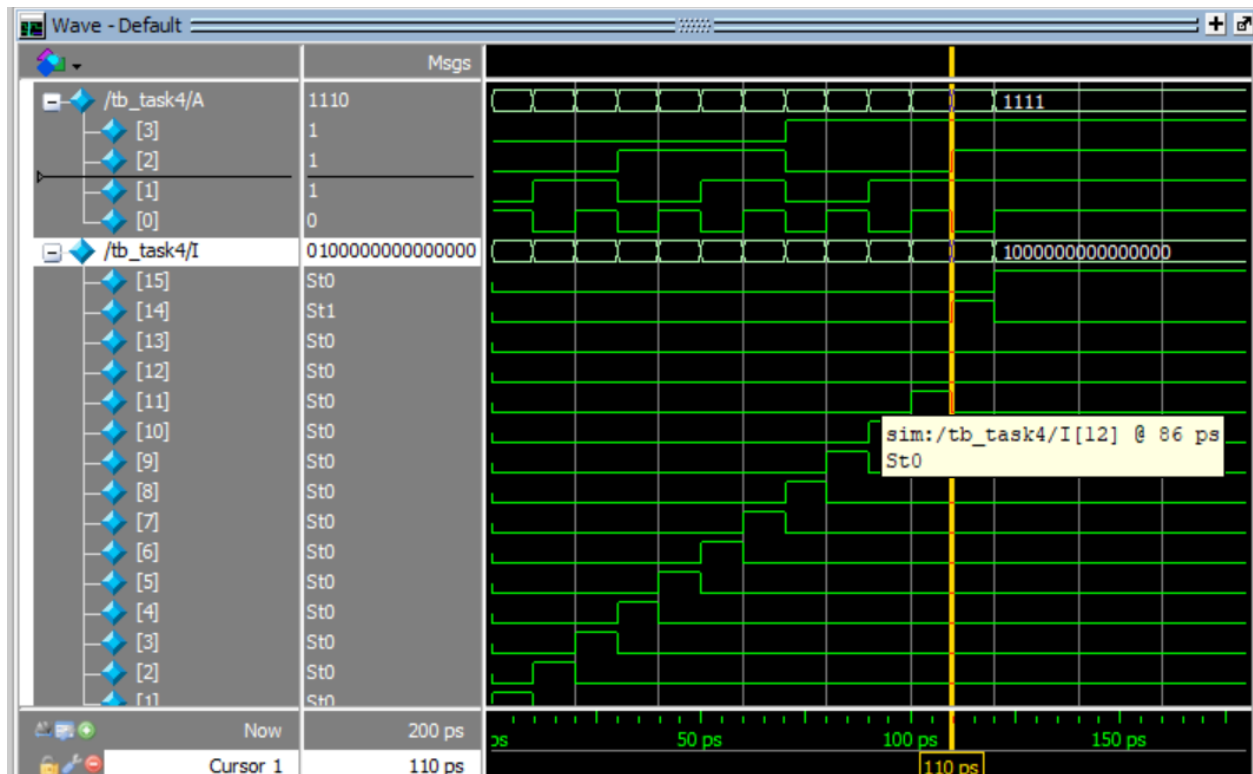

Conclusion:

In this lab, I learned how to implement Decoders using gate level modelling in Verilog.