

MULTIPLEXER IN VERILOG

LAB # 07



Fall 2023

CSE-304L Computer Organization and Architecture Lab

Submitted by: **Ali Asghar**

Registration No.: **21PWCSE2059**

Class Section: **C**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Submitted to:

Dr. Bilal Habib

Date:

7th December 2023


Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

ASSESSMENT RUBRICS COA LABS

LAB REPORT ASSESSMENT				
Criteria	Excellent	Average	Nil	Marks Obtained
1. Objectives of Lab	All objectives of lab are properly covered [Marks 10]	Objectives of lab are partially covered [Marks 5]	Objectives of lab are not shown [Marks 0]	
2. MIPS instructions with Comments and proper indentations.	All the instructions are well written with comments explaining the code and properly indented [Marks 20]	Some instructions are missing are poorly commented code [Marks 10]	The instructions are not properly written [Marks 0]	
3. Simulation run without error and warnings	The code is running in the simulator without any error and warnings [Marks 10]	The code is running but with some warnings or errors. [Marks 5]	The code is written but not running due to errors [Marks 0]	
4. Procedure	All the instructions are written with proper procedure [Marks 20]	Some steps are missing [Marks 10]	steps are totally missing [Marks 0]	
5. OUTPUT	Proper output of the code written in assembly [Marks 20]	Some of the outputs are missing [Marks 10]	No or wrong output [Marks 0]	
6. Conclusion	Conclusion about the lab is shown and written [Marks 20]	Conclusion about the lab is partially shown [Marks 10]	Conclusion about the lab is not shown[Marks0]	
7. Cheating			Any kind of cheating will lead to 0 Marks	
<p style="text-align: center;">Total Marks Obtained: _____</p> <p style="text-align: center;">Instructor Signature: _____</p>				

Task 1:

Implement 2X1 MUX in Verilog.

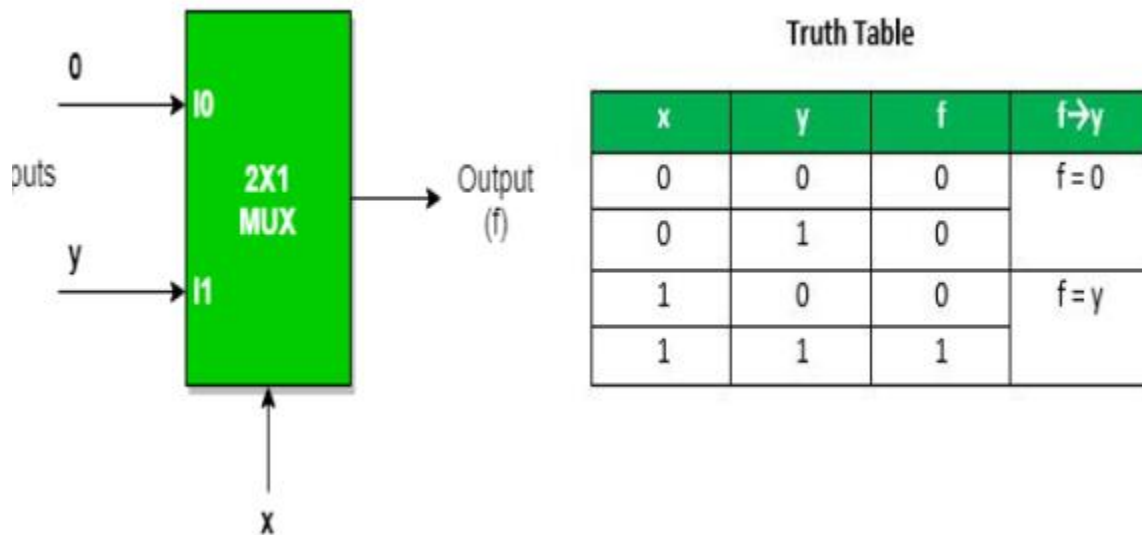

Code:



DUT Code:

```
1 module mux2x1(I, Sel, Out);
2     input [1:0] I;
3     input Sel;
4
5     output Out;
6     reg Out;
7
8     always@(I, Sel)
9         case(Sel)
10            1'b0 : Out = I[0];
11            1'b1 : Out = I[1];
12        endcase
13
14 endmodule
```

Test bench Code:


```
1  module tb_mux2x1();
2      reg [1:0] I;
3      reg Sel;
4      wire out;
5
6      mux2x1 my_mux2x1(I, Sel, out);
7
8      initial begin
9          I = 2'b00;
10         Sel = 0;
11         #10;
12
13         I = 2'b01;
14         Sel = 1;
15         #10;
16
17         I = 2'b10;
18         Sel = 1;
19         #10;
20     end
21
22 endmodule
```

Output:

 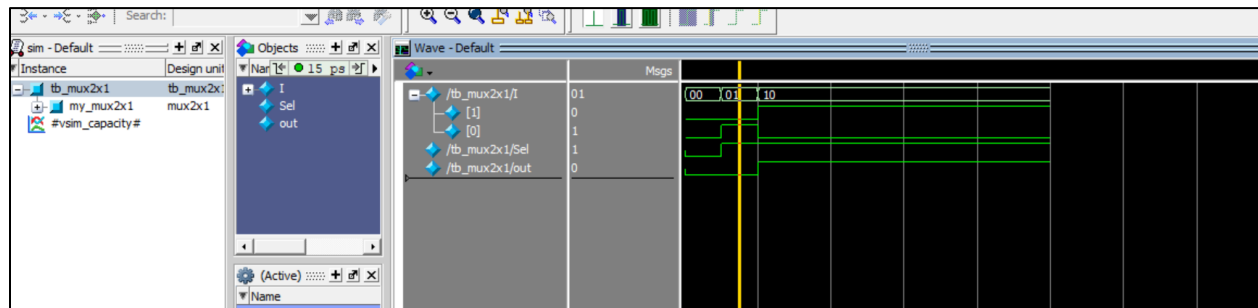

Task 2:

Implement 4X1 MUX using 2X1 MUX.

 

Code:


DUT Code:



```
task4.asm tb_mux2x1.v tb_demux.v tb_mux4x1.v mux_4x1.v mux2x1.v task2.v tb_task2.v task3.v tb_task3.v
1 module task2(I, Sel, Out);
2     input [3:0] I;
3     input [1:0] Sel;
4     wire O1, O2;
5     output Out;
6
7     mux2x1 mux1 ({I[1], I[0]}, Sel[0], O1);
8     mux2x1 mux2 ({I[3], I[2]}, Sel[0], O2);
9     mux2x1 mux3 ({O2, O1}, Sel[1], Out);
10
11 endmodule
12
13
```

Test bench Code:

```
Task4.asm  tb_mux2x1.v  tb_demux.v  tb_mux4x1.v  mux_4x1.v  mux2x1.v  task2.v  tb_task2.v  task3.v  tb_task3.v
1  module tb_task2();
2      reg [3:0] I;
3      reg [1:0] Sel;
4      wire out;
5      task2 my_mux4x1(I, Sel, out);
6
7      initial begin
8          I = 4'b0101;
9          Sel = 2'b00;
10         #10;
11
12         I = 4'b0101;
13         Sel = 2'b01;
14         #10;
15
16         I = 4'b0101;
17         Sel = 2'b10;
18         #10;
19
20         I = 4'b0101;
21         Sel = 2'b11;
22         #10;
23     end
```

Output:

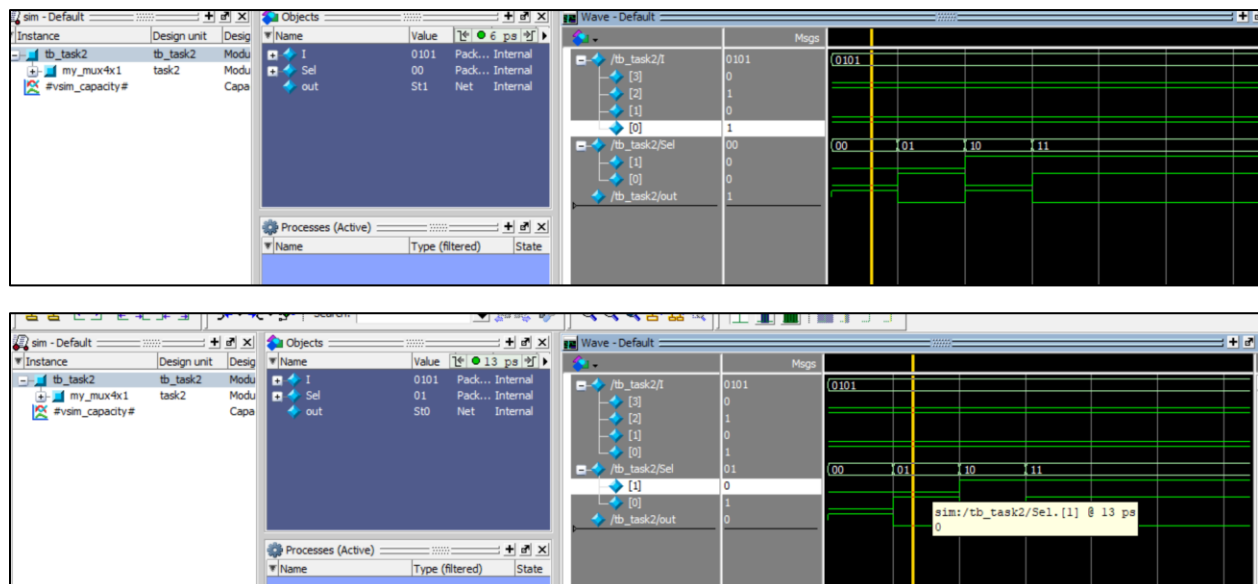

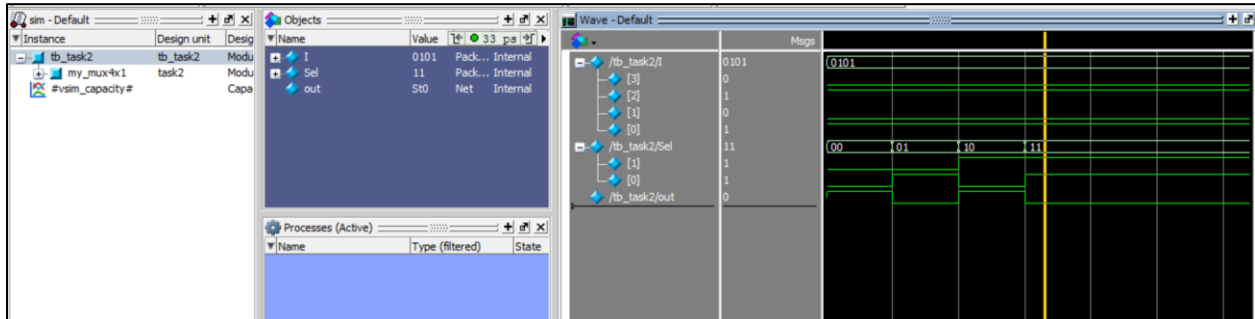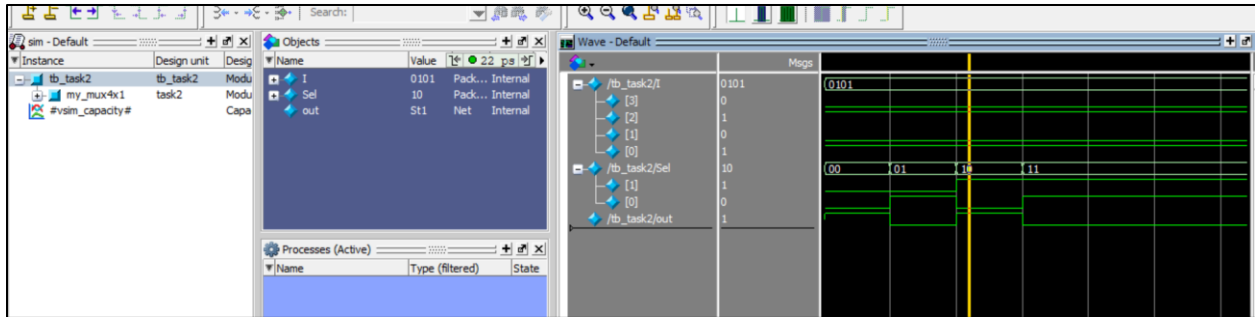

Task 3:

Design MUX where if the select to a MUX is 00 it will output A , 01 the output will be B , for 10 the output will be A+B and for 11 the output will be A-B.

Code:

DUT Code:

```

1  module task3(A, B, Sel, Out);
2      input [3:0] A;
3      input [3:0] B;
4      input [1:0] Sel;
5
6      output [3:0] Out;
7      reg [3:0] Out;
8
9      always@ (A, B, Sel)
10         case(Sel)
11             2'b00 : Out = A;
12             2'b01 : Out = B;
13             2'b10 : Out = A + B;
14             2'b11 : Out = A - B;
15         endcase
16     endmodule

```

Test bench Code:

```
Task4.asm  tb_mux2x1.v  tb_demux.v  tb_mux4x1.v  mux_4x1.v  mux2x1.v  task2.v  tb_task2.v  task3.v  tb_task3.v
1  module tb_task3();
2      reg [3:0] I1;
3      reg [3:0] I2;
4      reg [1:0] Sel;
5      wire [3:0] out;
6      task3 my_task3(I1, I2, Sel, out);
7
8  initial begin
9      I1 = 4'b1000;
10     I2 = 4'b0010;
11     Sel = 2'b00;
12     #10;
13
14     I1 = 4'b1000;
15     I2 = 4'b0010;
16     Sel = 2'b01;
17     #10;
18
19     I1 = 4'b1000;
20     I2 = 4'b0010;
21     Sel = 2'b10;
22     #10;
23
24     I1 = 4'b1000;
25     I2 = 4'b0010;
26     Sel = 2'b11;
27     #10;
28 end
29 endmodule
```


Output:

Wave - Default		Msgs			
+ /tb_task3/I1	1000	1000			
+ /tb_task3/I2	0010	0010			
+ /tb_task3/Sel	11	00	01	10	11
+ /tb_task3/out	0110	1000	0010	1010	0110

Conclusion:

In this lab, I learned how to implement Multiplexers using always statement (behavior level modelling) in Verilog.