

INTRODUCTION TO VERILOG

LAB # 06



Fall 2023

CSE-304L Computer Organization and Architecture Lab

Submitted by: **Ali Asghar**

Registration No.: **21PWCSE2059**

Class Section: **C**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Submitted to:

Dr. Bilal Habib

Date:

9th November 2023

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar


ASSESSMENT RUBRICS COA LABS

LAB REPORT ASSESSMENT				
Criteria	Excellent	Average	Nil	Marks Obtained
1. Objectives of Lab	All objectives of lab are properly covered [Marks 10]	Objectives of lab are partially covered [Marks 5]	Objectives of lab are not shown [Marks 0]	
2. MIPS instructions with Comments and proper indentations.	All the instructions are well written with comments explaining the code and properly indented [Marks 20]	Some instructions are missing are poorly commented code [Marks 10]	The instructions are not properly written [Marks 0]	
3. Simulation run without error and warnings	The code is running in the simulator without any error and warnings [Marks 10]	The code is running but with some warnings or errors. [Marks 5]	The code is written but not running due to errors [Marks 0]	
4. Procedure	All the instructions are written with proper procedure [Marks 20]	Some steps are missing [Marks 10]	steps are totally missing [Marks 0]	
5. OUTPUT	Proper output of the code written in assembly [Marks 20]	Some of the outputs are missing [Marks 10]	No or wrong output [Marks 0]	
6. Conclusion	Conclusion about the lab is shown and written [Marks 20]	Conclusion about the lab is partially shown [Marks 10]	Conclusion about the lab is not shown[Marks0]	
7. Cheating			Any kind of cheating will lead to 0 Marks	
<p style="text-align: center;">Total Marks Obtained: _____</p> <p style="text-align: center;">Instructor Signature: _____</p>				

Task 1:

Implement half adder in Verilog using gate level modeling.

Block and circuit diagram of half adder

 

Code:


DUT Code:

```
4bit_adder.v x half_adder.v x
1  module half_adder (A,B,S,C) ;
2
3      input A,B;
4      output C,S;
5      and a (C, A,B) ;
6      xor x (S, A,B) ;
7
8  endmodule
```

Test bench Code:


```
1 module tb_HA();
2     wire C, S;
3     reg A, B;
4     half_adder my_half_adder(A, B, C, S);
5
6 initial begin
7     A = 0;
8     B = 0;
9     #10;
10
11    A = 0;
12    B = 1;
13    #10;
14
15    A = 1;
16    B = 0;
17    #10;
18
19    A = 1;
20    B = 1;
21    #10;
22 end
23 endmodule
```

Output:

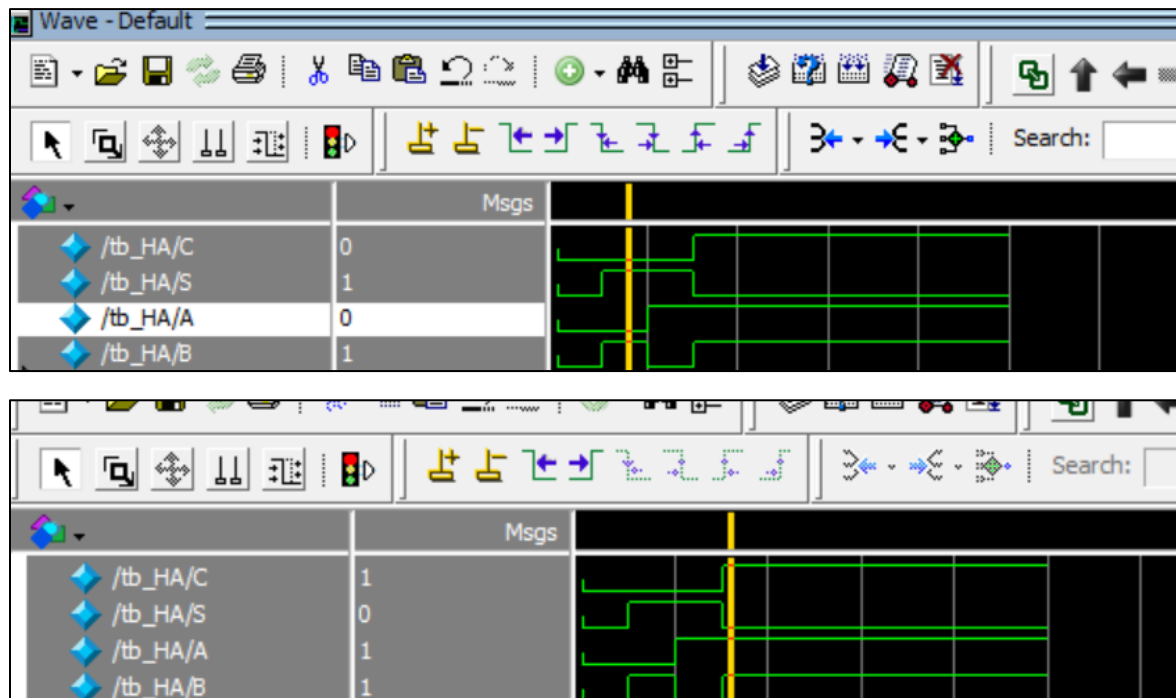

 Task 2:

Implement full adder using two half adder. (use the above half adder to create full adder)



Code:

DUT Code:

```
4bit_adder.v x half_adder.v x test_bench_HA.v x full_adder.v x
1  module full_adder(A,B,Cin,S,Cout) ;
2
3      input A,B,Cin;
4      output S,Cout;
5      wire sum1, carry1, carry2;
6
7      half_adder ha1(A, B, sum1, carry1);
8      half_adder ha2(Cin, sum1, S, carry2);
9      or o(Cout, carry1,carry2);
10
11  endmodule
12
```



Test bench Code:

```
1  module tb_FA();
2
3  wire C, S;
4  reg A, B , Cin;
5  full_adder my_full_adder(A, B, Cin, S , C);
6
7  initial begin
8
9      A = 0;
10     B = 0;
11     Cin = 0;
12     #10;
13
14     A = 0;
15     B = 0;
16     Cin = 1;
17     #10;
18
19     A = 0;
20     B = 1;
21     Cin = 0;
22     #10;
```

```
4bit_adder.v x half_adder.v x test_bench_HA.v x full_adder.v x test_bench_FA.v x
23
24     A = 0;
25     B = 1;
26     Cin = 1;
27     #10;
28
29     A = 1;
30     B = 0;
31     Cin = 0;
32     #10;
33
34     A = 1;
35     B = 0;
36     Cin = 1;
37     #10;
38
39     A = 1;
40     B = 1;
41     Cin = 0;
42     #10;
43
44     A = 1;
45     B = 1;
```


```
46     Cin = 1;
47     #10;
48     end
49
50 endmodule
51
```

Output:

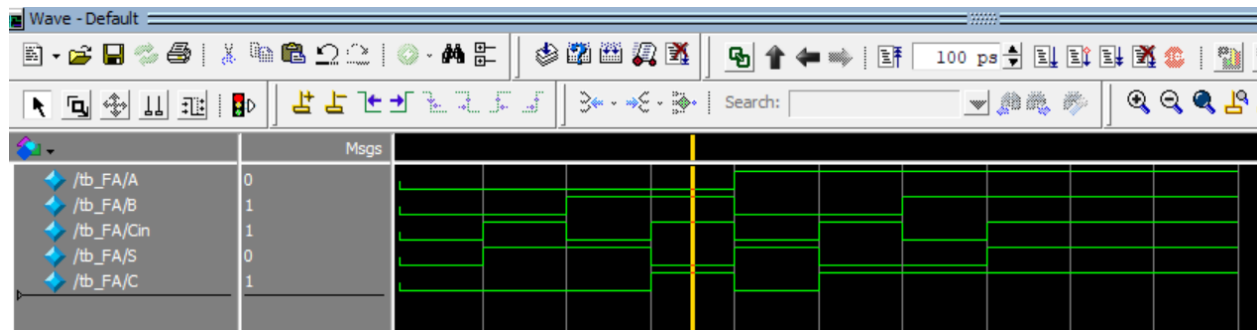 

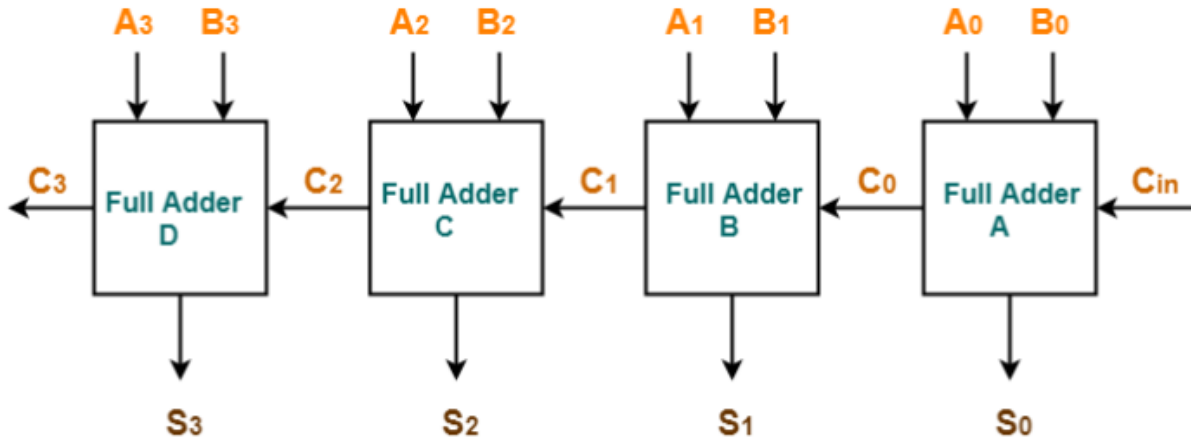Task 3:

Write a Verilog code for 4 bit ripple carry adder.



4-bit Ripple Carry Adder

Code:

DUT Code:

```
1  module four_bit_adder(in1, in2, Cin, S, Cout);
2
3      //input A0,A1,A2,A3, B0, B1, B2, B3,Cin;
4      input [3:0] in1, in2;
5      input Cin;
6      output [3:0] S;
7      output Cout;
8      wire carry1, carry2, carry3;
9
10     full_adder f1(in1[0], in2[0], Cin, S[0], carry1);
11     full_adder f2(in1[1], in2[1], carry1, S[1], carry2);
12     full_adder f3(in1[2], in2[2], carry2, S[2], carry3);
13     full_adder f4(in1[3], in2[3], carry3, S[3], Cout);
14
15
16 endmodule
17
```

Test bench Code:

```
half_adder.v x test_bench_HA.v x full_adder.v x test_bench_FA.v x 4bit_adder.v x test_bench_four_bit_adder.v x
1  module tb_four_bit_adder();
2      reg [3:0] in1, in2;
3      wire [3:0] S;
4      reg Cin;
5      wire Cout;
6
7      four_bit_adder my_four_bit_adder(in1, in2, Cin, S, Cout);
8
9
10  initial begin
11      in1 = 4'hA;
12      in2 = 4'hB;
13      Cin = 0;
14      #10;
15
16      in1 = 4'hA;
17      in2 = 4'hB;
18      Cin = 1;
19      #10;
20
21      in1 = 4'hC;
22      in2 = 4'hD;
23      Cin = 0;
24
25
26      in1 = 4'hA;
27      in2 = 4'hC;
28      Cin = 0;
29      #10;
30  end
31
32  endmodule
```

Output:

Wave - Default			Msgs							
Inputs			(Inputs)							
/tb_four_bit_adder/in1	1010		1010		1100		1010			
/tb_four_bit_adder/in2	1011		1011		1101		1100			
/tb_four_bit_adder/Cin	0									
Output			(Output)							
/tb_four_bit_adder/S	0101		0101		0110		1001		0110	
/tb_four_bit_adder/Cout	1									

Wave - Default			Msgs							
Inputs			(Inputs)							
/tb_four_bit_adder/in1	1100		1010		1100		1010			
/tb_four_bit_adder/in2	1101		1011		1101		1100			
/tb_four_bit_adder/Cin	0									
Output			(Output)							
/tb_four_bit_adder/S	1001		0101		0110		1001		0110	
/tb_four_bit_adder/Cout	1									

Conclusion:

In this lab, I learned about the basics of Verilog (Hardware Descriptive Language) in using ModelSim.