 


**A Taste of Data path + Control Design Example:
Factorial Circuit (Open Ended Lab)**

LAB # 11



Spring 2024

CSE-308L Digital System Design Lab

Submitted by: **Ali Asghar**

Registration No.: **21PWCSE2059**

Class Section: **C**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Submitted to:

Dr. Asif Ali Khan

Date:

1st June 2024

**Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar**

Objectives:


To implement a circuit that calculates factorial of a number.

Software used:


Xilinx ISE

Block Diagram:

The datapath for calculating the factorial of an “N” bit number is given below. The datapath is controlled by a Finite State Machine (FSM). FSM generates signals A_{sel} , A_{le} , B_{sel} and B_{le} at the correct times to operate the datapath. Input to FSM is a signal “Z” when $Z=0$ means the operation of the machine is complete and ANSWER can be read. The STG is also given in the following diagram.

 

State Transition Diagram:

 

I/O Connection:

Connect the input N to switches so automatically $N=8$ bits and connect the ANSWER to 8 LEDs. Don't give input greater than 5 else the ANSWER will not 8 bit wide.

Lab Task 1:

Factorial Datapath + Control Path Simulation

Code:

```
21 module testbench();
22     reg CLK = 0;
23     reg [7:0] data_in;
24     reg start;
25     wire done;
26     wire [7:0] out;
27     wire [2:0] state;
28
29     wire eqz, regN_sel, regN_en, tempFact_en, tempFact_sel, calc_Product, Ld_DC, dec_DC, product_done;
30
31     wire [7:0] regN_out;
32     wire [7:0] Decrementer_Out;
33     controller cp(CLK, eqz, start, product_done, regN_sel, regN_en, tempFact_en, tempFact_sel, Ld_DC, dec_DC,
34     factorial_datapath dp(eqz, product_done, regN_sel, regN_en, tempFact_en, tempFact_sel, Ld_DC, dec_DC,
35
36     always # 5 CLK = ~CLK;
37
38     assign regN_out = dp.regN_out;
39     assign Decrementer_Out = dp.Decrementer_Out;
40     initial begin
41         $monitor("%d, RegN=%d, RegTemp=%d, TempProduct=%d", $time, dp.regN_out, dp.tempFact_out, dp.temp_pr
42         data_in = 8'd4;
43         start = 1;
44     end
45 endmodule
```

Figure 1.1 testbench module

```
21 module controller (clk, eqz, start, product_done, regN_sel, regN_en, tempFact_en, tempFact_s, ^
22
23     input clk, eqz, start, product_done;
24
25     output reg regN_sel = 0 , regN_en = 0 , tempFact_en = 0 , tempFact_sel = 0 , Ld_DC = 0,
26     output reg [2:0] state;
27
28     parameter S0=3'b000, S1=3'b001, S2=3'b010, S3=3'b011, S4=3'b100, S5=3'b101, S6=3'b111;
29
30     always@(posedge clk) begin
31         case (state)
32             S0: if(start)
33                 state <= S1;
34             else
35                 state <= S0;
36
37             S1: state <= S2;
38             S2: state <= S3;
39             S3: #2
40                 if (product_done)
41                     state <= S4;
42             else
```

Figure 1.2.1: Control Path Code – Part 1

```

42         else
43             state <= S3;
44
45         S4: state <= S5 ;
46
47         S5: #2 if (eqz)
48             state <= S6;
49         else
50             state <= S2;
51         S6: state <= S6;
52         default: state <= S0;
53     endcase
54 end
55
56 // combinational logic to generate datapath control signals
57 always @(*) begin
58     case (state)
59         S0: begin regN_sel <= 0; regN_en <= 0; tempFact_en <= 0; tempFact_sel <= 0; Ld_DC = 0
60         S1: begin regN_sel <= 1; regN_en <= 1; tempFact_en <= 1; tempFact_sel <= 1; Ld_DC = 0
61         S2: begin regN_en <= 1; tempFact_en <= 1; Ld_DC = 0; dec_DC <= 0; calc_Product <= 0;
62         S3: begin regN_sel <= 0; regN_en <= 0; tempFact_en <= 0; tempFact_sel <= 0; Ld_DC = 0
63         S4: begin regN_sel <= 0; regN_en <= 0; tempFact_en <= 0; tempFact_sel <= 0; Ld_DC = 1

```

Figure 1.2.2: Control Path Code – Part 2

```

63         S4: begin regN_sel <= 0; regN_en <= 0; tempFact_en <= 0; tempFact_sel <= 0; Ld_DC = 1
64         S5: begin regN_sel <= 0; regN_en <= 0; tempFact_en <= 0; tempFact_sel <= 0; Ld_DC = 0
65         S6: begin regN_sel <= 0; regN_en <= 0; tempFact_en <= 0; tempFact_sel <= 0; Ld_DC = 0
66     endcase
67 end
68 endmodule

```

Figure 1.2.3: Control Path Code – Part 3

```

21 module factorial_datapath (eqz, product_done, regN_sel, regN_en, tempFact_en, tempFact_sel, Ld_DC, dec_DC,
22     input regN_sel, regN_en, tempFact_en, tempFact_sel, Ld_DC, dec_DC, calc_Product, clk;
23     input [7:0] data_in;
24     output eqz;
25     output [7:0] out;
26     output product_done;
27
28     wire [7:0] MUX1_OUT, MUX2_OUT, regN_out, tempFact_out, Decrementer_Out;
29     wire [7:0] temp_product;
30
31     Mux2x1 mux1(.out(MUX1_OUT) , .I0(Decrementer_Out), .I1(data_in), .s(regN_sel));
32     PIP01 A (regN_out, MUX1_OUT, regN_en, clk);
33
34     Mux2x1 mux2(.out(MUX2_OUT) , .I0(temp_product), .I1(1), .s(tempFact_sel));
35     PIP02 P (tempFact_out, MUX2_OUT, tempFact_en, clrTemp, clk);
36
37     DECREMENTER DC (Decrementer_Out, regN_out, Ld_DC, dec_DC, clk);
38     EQZ_COMP(eqz, regN_out);
39
40     multiplier mult(regN_out, tempFact_out, clk, calc_Product, product_done, temp_product);
41     PIP01 D(out, temp_product, output_en, clk);
42
43 endmodule

```

Figure 1.3: Factorial Datapath Code

```

module Mux2x1(out , I0, I1, s);
    input [7:0]I0 , I1 ;
    input s;
    output [7:0]out;

    assign out = (s) ? I1 : I0;

endmodule

```

Figure 1.4: 2x1 Multiplexer Code

```

module PIPO1 (dout, din, ld, clk);
    input [7:0] din;
    input ld, clk;
    output reg [7:0] dout;

    always @ (posedge clk)
        if (ld)
            dout <= din;
endmodule

```

Summary (out of date) × testbench.v × controller.v × product_datapath.v × PIPO1.v ×

Figure 1.5: Parallel In Parallel Out (PIPO) Register 1 Code

```

module PIPO2 (dout, din, ld, clr, clk);
    input [7:0] din;
    input ld, clr, clk;
    output reg [7:0] dout = 8'd0;

    always @ (posedge clk)
        if (clr)
            dout <= 8'b0;
        else if (ld)
            dout <= din;

endmodule

```

Summary (out of date) × testbench.v × controller.v × product_datapath.v × PIPO1.v × PIPO2.v ×

Figure 1.6: Parallel In Parallel Out (PIPO) Register 2 Code

```

21 module DECREMETER (dout, din, ld, dec, clk);
22     input [7:0] din;
23     input ld, dec, clk;
24     output reg [7:0] dout;
25
26     always @(posedge clk) begin
27         if (ld)
28             dout <= din;
29         else if (dec)
30             dout <= dout - 1;
31     end
32 endmodule

```

esign Summary x testbench.v x controller.v x product_datapath.v x Mux2x1.v x PIPO1.v x CNTR.v x

Figure 1.7: Decrementer Module Code

```

21 module EQZ (eqz, data);
22     input [7:0] data;
23     output eqz;
24     assign eqz = (data == 1);
25
26 endmodule
27

```

Figure 1.8: EQZ(Comparator) Module Code

```

21 module multiplier(
22     input [3:0] M,
23     input [3:0] Q,
24     input CLK,
25     input RST,
26     output reg product_done,
27     output reg [7:0] P = 8'd0
28 );
29     reg [3:0] A = 4'b0000;
30     reg [3:0] Q_reg;
31     reg [3:0] count = 4'b0000; // To count the number of shifts
32     reg C = 1'b0;
33
34     always @(posedge CLK) begin
35         if(~RST) begin
36             Q_reg = Q;
37             if(count > 0)
38                 count = 0;
39         end
40
41         else begin

```

mary (out of date) x testbench.v x controller.v x product_datapath.v x PIPO1.v x PIPO2.v x multiplier.v x

Figure 1.9.1: Unsigned 4-bit Multiplier Code – Part 1

```

42         if(count == 0) begin
43             product_done = 0;
44             Q_reg = Q;
45         end
46         if (count < 4) begin
47             if (Q_reg[0]) begin
48                 {C,A} = A + M;
49             end
50
51             Q_reg = {A[0], Q_reg[3:1]}; // Shift right and include A's LSB in Q
52             A = {C,A[3:1]};
53             count = count + 1;
54         end
55     end
56     if (count == 4) begin
57         P <= {A, Q_reg};
58         product_done = 1;
59     end
60 end
61 endmodule
62

```

mary (out of date) x testbench.v x controller.v x product_datapath.v x PIPO1.v x PIPO2.v x multiplier.v x

Figure 1.9.2: Unsigned 4-bit Multiplier Code – Part 2

Output:

 


Figure 1.10: Output Waveform of Factorial Datapath and Control path using 4-bit Multiplier (Output is saved in RegTemp register)

Lab Task 2:

Product Datapath + Control Path Simulation

Code:

```
21 module testbench();
22     reg CLK = 0;
23     reg [3:0]data_in_A;
24     reg [3:0]data_in_B;
25     reg start;
26     reg [2:0] state = 3'b000;
27     wire done;
28     wire [7:0]out;
29     wire eqz, LdA, LdB, LdP, clrp;
30
31     controller cp(CLK, eqz, start, LdA, LdB, LdP, clrp, done, state);
32     product_datapath dp(eqz, LdA, LdB, LdP, clrp, data_in_A, data_in_B, CLK);
33
34     always # 5 CLK = ~CLK;
35     assign out = dp.Z;
36
37     initial begin
38         data_in_A = 4'd10;
39         data_in_B = 4'd10;
40         #10
41         start = 1;
42     end
```

Figure 2.1 testbench module

```
21 module controller (clk, eqz, start, LdA, LdB, LdP, clrp, done, state);
22
23     input clk, eqz, start;
24
25     output reg LdA = 0 , LdB = 0 , LdP = 0 , clrp = 0 , done = 0;
26     output reg [2:0] state;
27     //reg [2:0] state;
28     parameter S0=3'b000, S1=3'b001, S2=3'b010, S3=3'b011, S4=3'b100;
29
30     always@(posedge clk) begin
31         case (state)
32             S0: if(start)
33                 state <= S1;
34                 else
35                     state <= S0;
36             S1: state <= S2;
37             S2: state <= S3;
38             S3: #2 if (eqz)
39                 state <= S4;
40                 else
41                     state <= S3;
42             S4: state <= S4;
43             default: state <= S0;
44         endcase
45     end
```

Design Summary (out of date)

testbench.v

controller.v

Figure 2.2.1: Product Control Path Code – Part 1

```

46
47 // combinational logic to generate datapath control signals
48 always @(*) begin
49     case (state)
50         S0: begin LdA = 0; LdB = 0; LdP = 0; clrp = 0; done = 0; end
51         S1: begin LdA = 1; LdB = 0; LdP = 0; clrp = 0; done = 0; end
52         S2: begin LdA = 0; LdB = 1; LdP = 0; clrp = 0; done = 0; end
53         S3: begin LdA = 0; LdB = 0; LdP = 1; clrp = 0; done = 0; end
54         S4: begin LdA = 0; LdB = 0; LdP = 0; clrp = 1; done = 1; end
55     endcase
56 end
57
58 endmodule
59
60

```

 


Figure 2.2.2: Product Control Path Code – Part 2

```

21 module product_datapath (eqz, LdA, LdB, Ldp, clrp, data_in_A, data_in_B, clk, out);
22     input LdA, LdB, Ldp, clrp, clk;
23     input [3:0] data_in_A;
24     input [3:0] data_in_B;
25     output eqz;
26     output [7:0] out;
27
28     wire [7:0] X, Y, Z;
29     PIPO1 A (X, data_in_A, LdA, clk);
30     PIPO2 B (Y, data_in_B, LdB, clrp, clk);
31
32     multiplier mult(X, Y, clk, Ldp, eqz, Z);
33
34     assign out = Z;
35
36 endmodule
37
38

```

 


Figure 2.3: Product Datapath Code

Output:

 


Figure 2.4: Output Waveform of Product Datapath and Control path using 4-bit Multiplier

 


Figure 2.5: Output Waveform of Product Datapath and Control path using 4-bit Multiplier