


Practice Quiz 2 & Solution

Q1.

Draw the logic circuit described by the Verilog code below.

```
module fun (x, y, z, f1, f2);  
  
    //module fun (x, y, a, b, c);  
    //This was the given ports list. You see the error.  
    //I did this on purpose once again.  
    /*I wanted to see if you read the problem carefully  
    before attempting it. After the error is fixed, you were  
    required to draw the logic diagram of the synthesized  
    hardware as shown in the solution below.*/  
  
    input x, y, z;  
    output f1, f2;  
  
    wire w1, w2;  
  
    xor x1 (w1, x, y);  
    not n1 (f1, w1);  
    and a1 (w2, f1, z);  
    or o1 (f2, w2, y);  
  
endmodule
```


****Solution****

 

//See HW1's Problem 1

 Q2.

BCD counters, also known as decade or MOD-10 counters, are often used whenever pulses are to be counted and the results displayed in decimal. A single BCD counter counts from 0 to 9 and then recycles to 0. To count a larger number than 9, we should cascade a multiple of BCD counters, one for each decade. For example, to construct a BCD counter operation that counts from 000 to 999 we need a three-BCD counter and should proceed with the following design:



1. Initially all counters are reset to 0.
2. Each input pulse advances the first counter once.
3. The 10th input pulse causes the first counter to recycle, which advances the second counter.
4. This continues until the second counter recycles, which advances the third counter.
5. The cycle repeats until 999 is reached and all three counters start again at zero.

In this problem you are required to design a **three_BCD counter** using as building block the BCD counter given below.

```
module BCD (CLOCK, CLR, Q);  
  
    input CLOCK, CLR; //Clock and Reset  
    output [3:0] Q; //BCD output  
    reg [3:0] Q;  
  
    always @(negedge CLOCK)  
        if (CLR | Q==4'd9)  
            Q <= 4'd0;  
        else  
            Q <= Q + 1;  
  
endmodule
```

Use the following module template for your **three_BCD**:

```
module three_BCD (CLOCK, CLR, BCDu, BCDt, BCDh);  
  
    input CLOCK, CLR;  
    output [3:0] BCDu, BCDt, BCDh; //u=1, t=10, h=100  
    //WRITE YOUR CODE HERE  
  
endmodule
```

****Solution****

```
module three_BCD (CLOCK, CLR, BCDu, BCDt, BCDh);  
  
    input CLOCK, CLR;  
    output [3:0] BCDu, BCDt, BCDh; //u=1, t=10, h=100  
    //WRITE YOUR CODE HERE  
  
    BCD c1 (CLOCK, CLR, BCDu[3:0]);  
    BCD c2 (BCDu[3], CLR, BCDt[3:0]);  
    BCD c3 (BCDt[3], CLR, BCDh[3:0]);  
  
endmodule
```

//Similar to HW3's Problems 2 & 8
