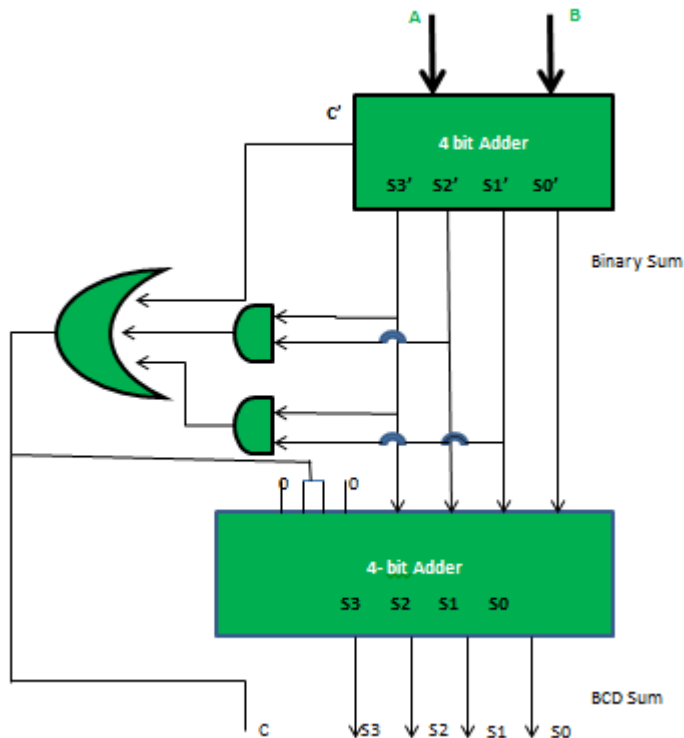


Name: _____

Registration: _____

Design a BCD adder using as building block the 4-bit binary adder shown below. Use the provided block diagram and skeleton file to implement the BCD adder.

```
module add4 (c, s, a, b);  
  
    output [3:0] s;  
    output c;  
    input [3:0] a, b;  
  
    assign {c, s} = a + b;  
  
endmodule
```



```
module bcd (c, s, a, b);  
  
    output [3:0] s;  
    output c;  
    input [3:0] a, b;  
    //Write your coder here  
  
endmodule
```